



PET ENGINEERING COLLEGE



An ISO 9001:2015 Certified Institution

Accredited by NAAC, Approved by AICTE, Recognized by Government of Tamil Nadu
and Affiliated to Anna University

DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING

UNIT - I

CLASS : S5 ECE

SUBJECT CODE : EC3551

**SUBJECT NAME : TRANSMISSION LINES AND RF
SYSTEMS**

REGULATION : 2021

02.08.23

Unit-1

Transmission line theory

General theory of transmission lines

Transmission line: Transmission of electrical signal from source to receiver.


Lumped parameters: R, L, C discrete point

Distributed parameter: R, L, C

Types of transmission line:

Open wire line =

cables 

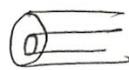co-axial line 

Primary constant

Resistance, $R (\Omega)$

Inductance, $L (H)$

Capacitance, $C (F)$


Conductance $G (\Omega^{-1})$

$Z \Rightarrow$ impedance $\Rightarrow R + j\omega L$

$Y \Rightarrow$ admittance $\Rightarrow G + j\omega C$

Transmission line Theory:

line of cascaded T section

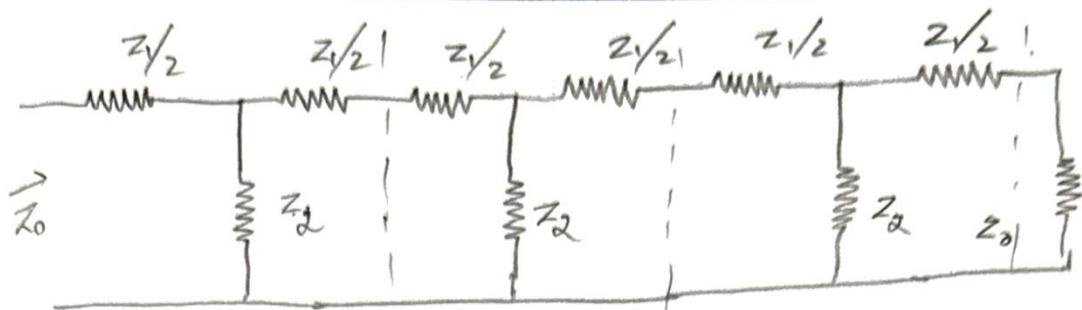

(i) Characteristic impedance:

$$Z_{OT} = \sqrt{Z_1 Z_2 \left(1 + \frac{Z_1}{4Z_2} \right)} \rightarrow (1)$$

$$Z_1 = Z \Delta x$$

$$Z_2 = \frac{1}{Y \Delta x}$$

Substitute in eqn (1)

$$Z_{OT} = \sqrt{\frac{Z \Delta x}{Y \Delta x} \left(1 + \frac{Z \Delta x}{4} \frac{1}{Y \Delta x} \right)} = \sqrt{\frac{Z}{Y} \left(1 + \frac{YZ (\Delta x)^2}{4} \right)}$$

Assume $\Delta x = 0$

$$Z_{OT} = \sqrt{\frac{Z}{Y}}$$

(ii) Propagation constant:

By Binomial theorem,

$$(a+b)^{1/2} = a + \frac{1}{2}b$$

$$\sqrt{\frac{Z_1}{Z_2} \left(1 + \frac{Z_1}{4Z_2} \right)} = \sqrt{\frac{Z_1}{Z_2} \left(1 + \frac{Z_1}{4Z_2} \right)^{1/2}}$$

$$= \sqrt{\frac{Z_1}{Z_2} \left(1 + \frac{1}{2} \times \frac{Z_1}{4Z_2} \right)} \rightarrow a$$

W.K.T. $e^y = 1 + \frac{y}{1} + \frac{y^2}{2} + \dots$

$$e^y = 1 + \frac{Z_1}{2Z_2} + \sqrt{\frac{Z_1}{Z_2} \left(1 + \frac{Z_1}{4Z_2} \right)} \rightarrow (b)$$

Sub (a) in (b)

$$e^{\gamma} = 1 + \frac{z_1}{2z_2} + \sqrt{\frac{z_1}{z_2}} + \frac{1}{8} \times \sqrt{\frac{z_1}{z_2}} \times \frac{z_1}{z_2}$$
$$= 1 + \frac{\sqrt{\frac{z_1}{z_2}}}{1!} + \frac{\left(\sqrt{\frac{z_1}{z_2}}\right)^2}{2!} + \frac{\left(\sqrt{\frac{z_1}{z_2}}\right)^3}{3!}$$

w.k.T

$$e^{\gamma} = 1 + \frac{\gamma}{1!} + \frac{\gamma^2}{2!} + \frac{\gamma^3}{3!} \rightarrow (d)$$

Compare (c) & (d)

$$\gamma = \sqrt{\frac{z_1}{z_2}}$$

By extended line Δx

$$z_1 = z \Delta x \quad z_2 = \frac{1}{y \Delta x}$$

$$\gamma = \sqrt{\frac{z \Delta x}{\frac{1}{y \Delta x}}}$$

$$\gamma = \sqrt{yz (\Delta x)^2}$$


if $\Delta x = 1$

$$\gamma = \sqrt{zy}$$

The transmission line general solution.

→ infinitesimal T-section

→ length (ds), current (I)

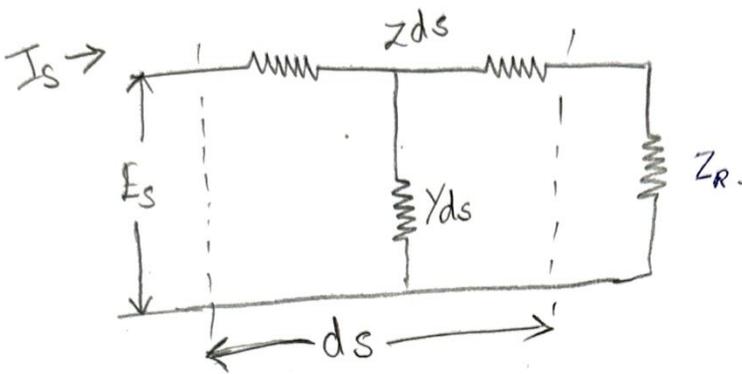

Voltage drop, $dE = I \cdot z ds$

$$\frac{dE}{ds} = I \cdot z \quad \rightarrow (1)$$

Current, $dI = E \cdot Y ds$

$$\frac{dI}{ds} = E \cdot Y \quad \rightarrow (2)$$

differentiate (1) & (2)

$$\frac{d^2 E}{ds^2} = z \frac{dI}{ds} = z \cdot E Y \quad \rightarrow (3)$$

$$\frac{d^2 I}{ds^2} = Y \frac{dE}{ds} = Y \cdot I Z \quad \rightarrow (4)$$

$$\frac{d^2}{ds^2} = m^2$$

$$m^2 E = Z E Y$$

$$m^2 E - Z E Y = 0$$

$$m^2 - Z Y = 0$$

Characteristic equation $m^2 = zy$ is given by

$$m = \sqrt{zy}$$

Solution of differential equation

$$E = Ae^{ms} + Be^{-ms}$$

$$I = Ce^{ms} + De^{-ms}$$

Sub m

$$E = Ae^{\sqrt{zy}s} + Be^{-\sqrt{zy}s} \rightarrow (5)$$

$$I = Ce^{\sqrt{zy}s} + De^{-\sqrt{zy}s} \rightarrow (6)$$

Condition: 1

$$s = 0, E = E_R, I = I_R \quad e^0 = 1$$

$$E_R = A + B \rightarrow (7)$$

$$I_R = C + D \rightarrow (8)$$

Differentiate (5) & (6) with respect to 's'

$$\frac{dE}{ds} = A \cdot \sqrt{zy} e^{\sqrt{zy}s} - B \sqrt{zy} e^{-\sqrt{zy}s}$$

$$\frac{dI}{ds} = C \sqrt{zy} e^{\sqrt{zy}s} - D \sqrt{zy} e^{-\sqrt{zy}s}$$

W.K.T

$$\frac{dE}{ds} = IZ, \quad \frac{dI}{ds} = EY$$

$$IZ = A \sqrt{zy} e^{\sqrt{zy}s} - B \sqrt{zy} e^{-\sqrt{zy}s}$$

$$I = A\sqrt{\frac{y}{z}} e^{\sqrt{zy}s} - B\sqrt{\frac{y}{z}} e^{-\sqrt{zy}s} \rightarrow (9)$$

$$EY = C\sqrt{zy}e^{\sqrt{zy}s} - D\sqrt{zy}e^{-\sqrt{zy}s}$$

$$E = C\sqrt{\frac{z}{y}} e^{\sqrt{zy}s} - D\sqrt{\frac{z}{y}} e^{-\sqrt{zy}s} \rightarrow (10)$$

Sub $s=0$, $E = E_r$, $I = I_r$ in eqn (9) & (10)

$$I_r = A\sqrt{\frac{y}{z}} - B\sqrt{\frac{y}{z}}$$

$$E_r = C\sqrt{\frac{z}{y}} - D\sqrt{\frac{z}{y}}$$

$$\sqrt{\frac{y}{z}} (A - B) = I_r$$

$$A - B = \sqrt{\frac{z}{y}} I_r \rightarrow (11)$$

$$\sqrt{\frac{z}{y}} (C - D) = E_r$$

$$C - D = \sqrt{\frac{y}{z}} E_r \rightarrow (12)$$

Adding (7) & (11)

$$A + B = E_r$$

$$A - B = \sqrt{\frac{z}{y}} I_r$$

$$2A = E_r + \sqrt{\frac{z}{y}} I_r$$

$$A = \frac{E_R}{2} + \sqrt{\frac{z}{y}} \frac{I_R}{2}$$

[(7) eqn]

$$E_R = A + B$$

$$E_R = \frac{E_R}{2} + \sqrt{\frac{z}{y}} \frac{I_R}{2} + B$$

$$\sqrt{\frac{z}{y}} = Z_0$$

$$= \frac{E_R}{2} + \frac{Z_0 I_R}{2} + B$$

$$\sqrt{y/z} = 1/Z_0$$

$$E_R = \frac{E_R + Z_0 I_R + 2B}{2}$$

$$2E_R = E_R + Z_0 I_R + 2B$$

$$E_R = Z_0 I_R + 2B$$

$$E_R - Z_0 I_R = 2B$$

$$B = \frac{E_R - Z_0 I_R}{2}$$

Adding (8) & (12)

$$I_R = C + D$$

$$\sqrt{\frac{y}{z}} E_R = C - D$$

$$I_R + \sqrt{\frac{y}{z}} E_R = 2C$$

$$C = \frac{I_R}{2} + \sqrt{\frac{y}{z}} \frac{E_R}{2}$$

$$C = \frac{I_R}{2} + \frac{1}{Z_0} \frac{E_R}{2}$$

Substitute C in eqn (8)

$$I_R = C + D$$

$$I_R = \frac{I_R}{2} + \frac{E_R}{2Z_0} + D$$

$$I_R = \frac{\cancel{I_R} + \cancel{E_R} + 2D}{2Z_0} \frac{I_R Z_0 + E_R + D 2Z_0}{2Z_0}$$

$$2I_R Z_0 = I_R Z_0 + E_R + 2D Z_0$$

$$I_R Z_0 = E_R + 2D Z_0$$

$$I_R Z_0 - E_R = 2D Z_0$$

$$D = \frac{I_R Z_0 - E_R}{2Z_0}$$

$$D = \frac{I_R}{2} - \frac{E_R}{2Z_0}$$

Take $\frac{E_R}{2}$ out in A & B

$$A = \frac{E_R}{2} \left[1 + \frac{Z_0 I_R}{2} \times \frac{2}{E_R} \right]$$

$$= \frac{E_R}{2} \left(1 + \frac{I_R Z_0}{E_R} \right)$$

$$\left[Z_R = \frac{E_R}{I_E} \right]$$

$$A = \frac{E_R}{2} \left(1 + \frac{Z_0}{Z_R} \right)$$

$$B = \frac{E_R}{2} \left(1 - \frac{I_R Z_0}{E_R} \right)$$

$$B = \frac{E_R}{2} \left(1 - \frac{Z_0}{Z_R} \right)$$

Taking $\frac{I_R}{2}$ out in C & D

$$C = \frac{I_R}{2} \left(1 + \frac{E_R}{Z_0 I_R} \right)$$

$$= \frac{I_R}{2} \left(1 + \frac{Z_R}{Z_0} \right)$$

$$D = \frac{I_R}{2} \left(1 - \frac{Z_R}{Z_0} \right)$$

$$E = A e^{\sqrt{z} y s} + B e^{-\sqrt{z} y s}$$

$$= \frac{E_R}{2} \left(1 + \frac{Z_0}{Z_R} \right) e^{\sqrt{z} y s} + \frac{E_R}{2} \left(1 - \frac{Z_0}{Z_R} \right) e^{-\sqrt{z} y s}$$

$$I = C e^{\sqrt{z} y s} + D e^{-\sqrt{z} y s}$$

$$= \frac{I_R}{2} \left(1 + \frac{E_R}{Z_0 I_R} \right) e^{\sqrt{z} y s} + \frac{I_R}{2} \left(1 - \frac{Z_R}{Z_0} \right) e^{-\sqrt{z} y s}$$

$$= \frac{I_R}{2} \left(1 + \frac{Z_R}{Z_0} \right) e^{\sqrt{z} y s} + \frac{I_R}{2} \left(1 - \frac{Z_R}{Z_0} \right) e^{-\sqrt{z} y s}$$

04.08.23

Physical Significance of Transmission Line: Infinite line

$$E = \frac{E_R}{2} \left(1 + \frac{Z_0}{Z_R} \right) e^{\sqrt{ZY}S} + \frac{E_R}{2} \left(1 - \frac{Z_0}{Z_R} \right) e^{-\sqrt{ZY}S}$$

$$I = \frac{I_R}{2} \left(1 + \frac{Z_R}{Z_0} \right) e^{\sqrt{ZY}S} + \frac{I_R}{2} \left(1 - \frac{Z_R}{Z_0} \right) e^{-\sqrt{ZY}S}$$

$$E = \frac{E_R}{2} e^{\sqrt{ZY}S} + \frac{E_R}{2} \frac{Z_0}{Z_R} e^{\sqrt{ZY}S} + \frac{E_R}{2} e^{-\sqrt{ZY}S} - \frac{E_R}{2} \frac{Z_0}{Z_R} e^{-\sqrt{ZY}S}$$

$$= \frac{E_R}{2} \left(e^{\sqrt{ZY}S} + e^{-\sqrt{ZY}S} \right) + \frac{E_R}{2} \frac{Z_0}{Z_R} \left(e^{\sqrt{ZY}S} - e^{-\sqrt{ZY}S} \right)$$

$$\cosh x = \frac{e^x + e^{-x}}{2}$$

$$\sinh x = \frac{e^x - e^{-x}}{2}$$

$$\gamma = \sqrt{ZY}$$

$$E = E_R \cosh \gamma S + \frac{E_R Z_0}{Z_R} \sinh \gamma S$$

$$E = E_R \left[\cosh \gamma S + \frac{Z_0}{Z_R} \sinh \gamma S \right]$$

$$I = \frac{I_R}{2} e^{\sqrt{ZY}S} + \frac{I_R Z_R}{2 Z_0} e^{\sqrt{ZY}S} + \frac{I_R}{2} e^{-\sqrt{ZY}S} - \frac{I_R Z_R}{2 Z_0} e^{-\sqrt{ZY}S}$$

$$I = \frac{I_R}{2} \left[e^{\sqrt{z}ys} + e^{-\sqrt{z}ys} \right]$$

$$\frac{I_R Z_R}{2Z_0} \left[e^{\sqrt{z}ys} - e^{-\sqrt{z}ys} \right]$$

$$= \frac{I_R}{2} 2 \cosh \gamma_s + \frac{I_R Z_R}{2Z_0} 2 \sinh \gamma_s$$

$$I = I_R \left[\cosh \gamma_s + \frac{Z_R}{Z_0} \sinh \gamma_s \right]$$

At point $s=l$ $\rightarrow E = E_s$, $I = I_s$

$$E_s = E_R \left[\cosh \gamma l + \frac{Z_0}{Z_R} \sinh \gamma l \right]$$

$$\frac{I_s}{s} = I_R \left[\cosh \gamma l + \frac{Z_R}{Z_0} \sinh \gamma l \right]$$

$$Z_s = \frac{E_s}{I_s}$$

Case (i) if $Z_R = Z_0$

$$E_s = E_R \left[\cosh \gamma l + \frac{Z_0}{Z_0} \sinh \gamma l \right]$$

$$I_s = I_R \left[\cosh \gamma l + \sinh \gamma l \right]$$

$$Z_s = \frac{E_s}{I_s} = \frac{E_R \left[\cosh \gamma l + \sinh \gamma l \right]}{I_R \left[\cosh \gamma l + \sinh \gamma l \right]}$$

$$Z_s = Z_R$$

$$\text{if } Z_S = Z_R$$

$$Z_0 = Z_S$$

case ii) if $Z_R \neq Z_0$

$$Z_S = \frac{E_S}{I_S} = \frac{E_R \left[\cosh \gamma l + \frac{Z_0}{Z_R} \sinh \gamma l \right]}{I_R \left[\cosh \gamma l + \frac{Z_R}{Z_0} \sinh \gamma l \right]}$$

$$= \frac{Z_R \left[\frac{Z_R \cosh \gamma l + Z_0 \sinh \gamma l}{Z_R} \right]}{\left[\frac{Z_0 \cosh \gamma l + Z_R \sinh \gamma l}{Z_0} \right]}$$

$$Z_S = \frac{Z_0 (Z_R \cosh \gamma l + Z_0 \sinh \gamma l)}{Z_0 \cosh \gamma l + Z_R \sinh \gamma l}$$

Wavelength and Velocity of propagation -
infinite line.

Wavelength:

$$\lambda \propto \frac{1}{\beta} \text{ (phase constant)}$$

wavelength is inversely proportional
to phase constant

$$\lambda = \frac{2\pi}{\beta}$$

Velocity:

velocity is defined as the ratio of
angular frequency (ω) to phase constant (β)

$$V = \frac{\omega}{\beta}$$

$$Y = \sqrt{ZY}$$

$$Z = R + j\omega L$$

$$Y = \alpha + j\beta \rightarrow (1)$$

$$Y = G + j\omega C$$

$$Y = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$= \sqrt{RG + j\omega RC + j\omega LG - \omega^2 LC}$$

$$Y = \sqrt{RG - \omega^2 LC + j\omega(RC + LG)} \rightarrow (2)$$

Equate (1) & (2)

$$\alpha + j\beta = \sqrt{RG - \omega^2 LC + j\omega(RC + LG)}$$

$$(\alpha + j\beta)^2 = RG - \omega^2 LC + j\omega(RC + LG)$$

$$\alpha^2 - \beta^2 + 2\alpha\beta j = RG - \omega^2 LC + j\omega(RC + LG)$$

Equating real part

$$\alpha^2 - \beta^2 = RG - \omega^2 LC \rightarrow (3)$$

Imaginary part.

$$2\alpha\beta = (RC + LG)\omega$$

$$\alpha = \frac{\omega(RC + LG)}{2\beta}$$

Sub α in eqn (3)

$$\frac{\omega^2(RC + LG)^2}{4\beta^2} = \beta^2 = RG - \omega^2 LC$$

$$\times \frac{\omega^2(RC + LG)^2 - 4\beta^4}{4\beta^2} = RG - \omega^2 LC$$

$$\text{If } R = G = 0$$

$$-\beta^2 = -\omega^2 LC$$

$$\beta = \sqrt{\omega^2 LC}$$

$$\beta = \omega \sqrt{LC}$$

$$\lambda = \frac{2\pi}{\beta} = \frac{2\pi}{\omega \sqrt{LC}} \text{ m}$$

$$V = \frac{\omega}{\beta} = \frac{\omega}{\omega \sqrt{LC}}$$

$$V = \frac{1}{\sqrt{LC}} \text{ ms}^{-1}$$

Waveform distortion:

There are two types,

- i) frequency distortion
- ii) phase distortion

Frequency distortion:

When the signal has more than one frequency, signals are not attenuated then it is called frequency distortion

Phase distortion: ^(delay)

When the signal has more than one frequency the signals are not transmitted equally, a delay is introduced between these signals which leads to phase distortion.

07.08.23 Distortionless lines:

⇒ If a line is said to be distortionless lines, the α and velocity (v) is independent of frequency,

⇒ The condition of distortionless line

$$LG = RC$$

$$\beta_0 = \sqrt{ZY}$$

$$Z = R + j\omega L$$

$$Y = G + j\omega C$$

$$Y = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$= \sqrt{RG + j\omega RC + j\omega LG + j^2\omega^2 LC}$$

$$= \sqrt{RG + j\omega RC + j\omega LG + j^2\omega^2 LC}$$

$$= \sqrt{RG + j^2\omega^2 RC + 2j\omega RC}$$

$$RG = (\sqrt{RG})^2$$

$$j^2\omega^2 LC = (\sqrt{j^2\omega^2 LC})^2 \text{ - } j^2 \text{ - } j^2 \text{ - } j^2$$

$$= \sqrt{(\sqrt{RG})^2 + (\sqrt{j^2\omega^2 LC})^2 + 2j\omega RC}$$

$$= \sqrt{(\sqrt{RG})^2 + (\sqrt{j^2\omega^2 LC})^2 + 2j\omega \sqrt{RC} \sqrt{RC}}$$

$$= \sqrt{(\sqrt{RG})^2 + (\sqrt{j^2\omega^2 LC})^2 + 2j\omega \sqrt{RC} \sqrt{LC}}$$

$$= \sqrt{(\sqrt{RG})^2 + (\sqrt{j^2\omega^2 LC})^2 + 2j\omega \sqrt{RG} \sqrt{LC}}$$

$$= \sqrt{(\sqrt{RG} + \sqrt{j^2\omega^2 LC})^2}$$

$$Y = \sqrt{RG} + j\omega \sqrt{LC}$$

$$Y = \alpha + j\beta$$

$$\alpha = \sqrt{RG}$$

$$\beta = \omega\sqrt{LC}$$

$$v = \frac{\omega}{\beta} = \frac{\omega}{\omega\sqrt{LC}}$$

$$= \frac{1}{\sqrt{LC}}$$

Here α & v are independent of frequency.

Loading of lines:

\Rightarrow In order to achieve distortionless lines, the ratio of L/C should be increased.

\Rightarrow It is done by increasing inductance (L) in transmission line by inserting inductance (L) in series. This is called loaded lines. This loading coil is called lumped inductor.

Telephone Cable, (distorted line)

* twisted pair cable (insulated)

* audio frequency $\boxed{L = G = 0}$

$$V = \sqrt{ZY}$$

$$Z = R + j\omega L$$

$$Y = G + j\omega C$$

$$Y = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$Y = \sqrt{(R + 0)(0 + j\omega C)}$$

$$Y = \sqrt{j\omega RC}$$

$$(1 + j)^2 = 1 + j^2 + 2j \\ = 1 - 1 + 2j$$

$$Y = \sqrt{2 \times \frac{j\omega RC}{2}}$$

$$(1 + j)^2 = 2j \\ 1 + j = \sqrt{2j}$$

$$= (1 + j) \sqrt{\frac{\omega RC}{2}}$$

$$\alpha + j\beta = \sqrt{\frac{\omega RC}{2}} + j\sqrt{\frac{\omega RC}{2}}$$

$$\alpha = \sqrt{\frac{\omega RC}{2}} \quad \beta = \sqrt{\frac{\omega RC}{2}}$$

$$V = \frac{\omega}{\beta} = \frac{\omega\sqrt{2}}{\sqrt{\omega RC}}$$

$$V = \sqrt{\frac{2\omega}{RC}}$$

Now analyze it by product method

1.23 Types of loading:

- i) Inductance loading
- ii) Continuous loading
- iii) Patch loading

Inductance loading:

In this, inductance (L) is increased by introducing of loading coils at uniform interval.

Continuous loading

Iron or other magnetic material is wound on transmission line to increase permeability of surrounding to increase inductance.

Patch loading:

It employs section of loaded cable which is separated by unloaded cable.

Inductance loading of telephone cable:

In order to make telephone cable as distortionless cable, it is

necessary to increase the inductance (L) and keep $G=0$. Increasing the inductance is called inductance loading.

$$Y = \sqrt{ZY}$$

$$Z = R + j\omega L$$

$$Y = G + j\omega C$$

$$Z = |Z| \cdot \angle Z$$

$$= \sqrt{R^2 + \omega^2 L^2} \cdot \tan^{-1}\left(\frac{\omega L}{R}\right)$$

$$= \sqrt{R^2 + \omega^2 L^2} \left(\frac{\pi}{2} - \tan^{-1}\left(\frac{R}{\omega L}\right) \right)$$

$$Y = |Y| \cdot \angle Y$$

$$= \sqrt{\omega^2 C^2} \tan^{-1}\left(\frac{\omega C}{0}\right)$$

$$= \omega C \tan^{-1}(\infty)$$

$$= \frac{\pi}{2} \omega C$$

$$\tilde{Z} = \sqrt{R^2 + \omega^2 L^2} \left(\frac{\pi}{2} - \tan^{-1}\left(\frac{R}{\omega L}\right) \rightarrow 0 \right)$$

$$Y = \frac{\pi}{2} \omega C \rightarrow (2)$$

$$\gamma = \sqrt{ZY}$$

$$= \sqrt{\sqrt{\omega^2 L^2} \left(1 + \frac{R^2}{\omega^2 L^2}\right)^{1/2} \left[\frac{\pi}{2} - \tan^{-1}\left(\frac{R}{\omega L}\right)\right]}$$

$$\sqrt{\frac{\pi}{2} \omega L}$$

$$= \sqrt{\omega^2 LC \left(1 + \frac{R^2}{\omega^2 L^2}\right)^{1/2} \left[\frac{\pi}{2} - \tan^{-1}\left(\frac{R}{\omega L}\right)\right]}$$

$$= \omega \sqrt{LC} \left[1 + \frac{R^2}{\omega^2 L^2}\right]^{1/2} \left[\frac{\pi}{2} - \tan^{-1}\left(\frac{R}{\omega L}\right)\right]^{1/2}$$

$\frac{R^2}{\omega^2 L^2}$ is small

$$= \omega \sqrt{LC} \frac{\left[\frac{\pi}{2} - \tan^{-1}\left(\frac{R}{\omega L}\right)\right]^{1/2}}{2} \quad \text{as } \frac{1}{2} = \frac{1}{2}$$

$$\gamma = \omega \sqrt{LC} \left[\frac{\pi}{2} - \frac{1}{2} \tan^{-1}\left(\frac{R}{\omega L}\right)\right] \rightarrow (3)$$

$$\underline{\gamma} = |\gamma| \angle \theta \quad ; \quad e^{j\theta} = \cos\theta + j\sin\theta$$

$$\gamma = |\gamma| e^{j\theta} \rightarrow (4)$$

$$\theta = \frac{\pi}{2} - \tan^{-1}\left(\frac{R}{\omega L}\right) \rightarrow (5)$$

Taking cos on both sides

$$\cos \theta = \cos \left(\frac{\pi}{2} - \frac{1}{2} \tan^{-1} \left(\frac{R}{\omega L} \right) \right)$$

$$= \sin \left(\frac{1}{2} \tan^{-1} \left(\frac{R}{\omega L} \right) \right)$$

$$= \frac{1}{2} \tan^{-1} \left(\frac{R}{\omega L} \right)$$

$$\cos \theta = \frac{1}{2} \frac{R}{\omega L}$$

Taking sine of both sides (5)

$$\sin \theta = \sin \left[\frac{\pi}{2} - \frac{1}{2} \tan^{-1} \left(\frac{R}{\omega L} \right) \right]$$

$$= \cos \left(\frac{1}{2} \tan^{-1} \left(\frac{R}{\omega L} \right) \right)$$

$$\sin \theta = 1$$

$$e^{j\theta} = \cos \theta + j \sin \theta$$

$$e^{j\theta} = \frac{1}{2} \frac{R}{\omega L} + j$$

$$\gamma = |\gamma| \angle \gamma = \omega \sqrt{LC} \left(\frac{R}{2\omega L} + j \right)$$

$$\gamma = \omega \sqrt{LC} \left(\frac{R}{2\omega L} + j \right)$$

$$\gamma = \frac{\omega \sqrt{LC} R}{2\omega L} + \omega \sqrt{LC} j$$

$$\begin{aligned} \theta \text{ is small} \\ \cos \theta &= 1 \\ \sin \theta &= \tan \theta = \theta \\ \tan^{-1} \theta &= \theta \end{aligned}$$

$$\begin{aligned} \cos 90^\circ - \theta &= \sin \theta \\ \sin 90^\circ - \theta &= \cos \theta \end{aligned}$$

$$\alpha + j\beta = \frac{R}{2} \sqrt{\frac{C}{L}} + j\omega\sqrt{LC}$$

$$\alpha = \frac{R}{2} \sqrt{\frac{C}{L}}$$


$$\beta = \omega\sqrt{LC}$$

$$v = \frac{\omega}{\beta} = \frac{\omega}{\omega\sqrt{LC}} = \frac{1}{\sqrt{LC}}$$

Since, α and v are independent of frequency, the inductance loading makes the telephone cable as distortion less line (a) cable.

14.08.23

Campbell's Equation

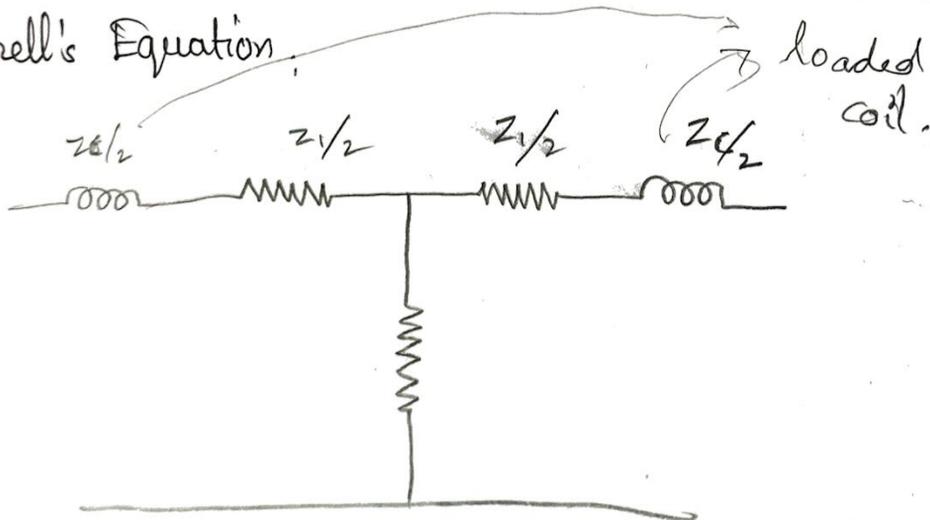

$$\frac{Z_1'}{2} = \frac{Z_0}{2} + \frac{Z_1}{2}$$

$$\frac{Z_1}{2} = Z_0 \frac{\tan \gamma l}{2}$$

$$Z_2 = \frac{Z_0}{\sin \gamma l}$$

$$\cosh \gamma l' = 1 + \frac{Z_1'}{Z_2}$$

$$= 1 + \frac{\left(\frac{Z_c}{2} + \frac{Z_1}{2} \right)}{Z_2}$$

$$= 1 + \frac{\left(\frac{Z_c}{2} + \frac{Z_0 \tan \gamma l}{2} \right)}{\frac{Z_0}{\sinh \gamma l}}$$

$$= 1 + \frac{Z_c}{2} \frac{Z_0 / \sinh \gamma l}{Z_0 / \sinh \gamma l} + \frac{Z_0 \tanh \gamma l}{2} \frac{Z_0 / \sinh \gamma l}{Z_0 / \sinh \gamma l}$$

$$= 1 + \frac{Z_c \sinh \gamma l}{2 Z_0} + \frac{\tanh \gamma l \cdot \sinh \gamma l}{2}$$

$$= 1 + \frac{Z_c \sinh \gamma l}{2 Z_0} + \frac{(\cosh \gamma l - 1) \times \sinh \gamma l}{\sinh \gamma l}$$

$$= 1 + \frac{Z_c}{2 Z_0} \sinh \gamma l + \cosh \gamma l - 1$$

$$\left[\frac{\tanh \gamma l}{2} = \frac{(\cosh \gamma l - 1)}{\sinh \gamma l} \right]$$

$$\cosh \gamma l' = \frac{Z_c}{2 Z_0} \sinh \gamma l + \cosh \gamma l$$

This is known as Campbell's equation

Inductance of a line not terminated by Z_0 .

Waveform transfers from source to load $\rightarrow e^{\gamma s}$

Waveform transfer from load to source then it is denoted as $e^{-\gamma s}$

$$Z_s = Z_0 \left[\frac{e^{\gamma s} + e^{-\gamma s} \left[\frac{Z_r - Z_0}{Z_r + Z_0} \right]}{e^{\gamma s} - e^{-\gamma s} \left[\frac{Z_r - Z_0}{Z_r + Z_0} \right]} \right]$$

(i) When the load impedance is terminated by characteristic impedance, then the input impedance is equal to characteristic impedance.


$$Z_r = Z_0$$

$$\boxed{Z_s = Z_0}$$

(ii) When load impedance is terminated by characteristic impedance, the signals are absorbed in the load.

and signals are not reflected. Hence this line is called a smooth line.

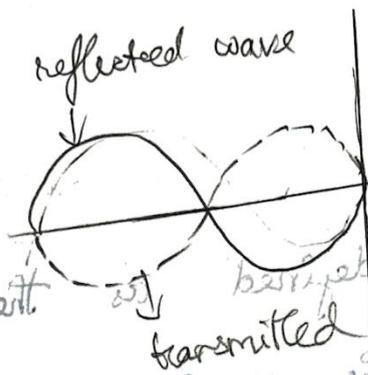ii) When load impedance is not terminated by characteristic impedance, there is reflection and transmission wave. And this reflected and transmitted wave constitute a standing wave.



Reflection coefficient: It is defined as a ratio of reflected voltage to incident voltage at the receiving end of the line.

$$K_r = \frac{Z_L - Z_0}{Z_L + Z_0}$$

(i) $Z_L = Z_0$; no reflection
 $K_r = 0$

(ii) $K_r = 0$

$K = -1$; out of phase 180°

$$\text{iii} / Z_r = \infty$$

$$R = \frac{Z_r - Z_0}{Z_r}$$

$$\frac{Z_r + Z_0}{Z_r}$$

$$= 1 - \frac{Z_0}{Z_r} / 1 + \frac{Z_0}{Z_r}$$

$$\frac{1}{\infty} = 0$$

$$= 1 = \angle 0^\circ \text{ (in phase)}$$

08.25

Return loss:

It is defined as the ratio of power at the receiving node to the power which is reflected at load.

$$\text{Return loss} = 20 \log \left| \frac{Z_r + Z_0}{Z_r - Z_0} \right|$$

Reflection loss

If $Z_r \neq Z_0$, reflection takes place. The power delivered to the load is less than the impedance matching, this reflection results in power loss. This loss is known as reflection loss.

$$\text{Reflection loss} = \ln \left[\frac{Z_R + Z_0}{2\sqrt{Z_0 Z_R}} \right] \text{ nepers or decibel (dB)}$$

Reflection factor:

Reflection factor indicates the change in current in the load due to reflection at the mismatched junction, (condition).

The ratio of current actually flowing in the load to the current that might flow under mismatched condition known as reflection factor.

$$\text{Reflection factor, } k = \frac{2\sqrt{Z_0 Z_R}}{(Z_R + Z_0)}$$

Input impedance & transmission impedance in transmission line - Open & Short circuited line

$$Z_S = Z_0 \frac{[Z_R \cosh \gamma l + Z_0 \sinh \gamma l]}{Z_0 \cosh \gamma l + Z_R \sinh \gamma l} \rightarrow (1)$$

(i) Open circuited Condition

$$Z_R = \infty ; Z_S = Z_{oc}$$

$$Z_{oc} = \frac{Z_0 [\cosh \gamma l + 0]}{[\sinh \gamma l]}$$

gives us that $Z_{oc} = \frac{Z_0}{\tanh \gamma l}$

etc. with load with a resistance is not short circuited condition:

$$Z_R = 0 ; Z_S = Z_{sc}$$

find the voltage across it

$$Z_{sc} = \frac{Z_0 [0 + Z_0 \sinh \gamma l]}{Z_0 \cosh \gamma l + 0}$$

$$= \frac{Z_0 \cancel{Z_0} \sinh \gamma l}{Z_0 \cosh \gamma l}$$

$$Z_{sc} = Z_0 \tanh \gamma l$$

$$Z_{sc} \cdot Z_{oc} = Z_0 \tanh \gamma l \times \frac{Z_0}{\tanh \gamma l}$$

$$Z_{sc} Z_{oc} = Z_0^2$$

$$Z_0 = \sqrt{Z_{sc} Z_{oc}}$$

$$\frac{Z_{oc}}{Z_{sc}} = \frac{Z_0}{\tanh \gamma l} = \frac{Z_0}{Z_0 \tanh^2 \gamma l}$$

$$\frac{Z_{oc}}{Z_{sc}} = \frac{1}{\tan^2 h \gamma l}$$

$$\tan^2 h \gamma l = \frac{Z_{sc}}{Z_{oc}}$$

$$\gamma l = \tan^{-2} h \left(\frac{Z_{sc}}{Z_{oc}} \right)$$